



## Voltage Regulator Design.

TI 77633 IC

- 5V input from  $\mu C$  to 3.3 (exact) output.
- Max  $I_{out} = 500\text{ mA}$ !

→ Breakout board built with soldered chip.


### Breakout Board (which is top)

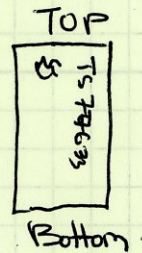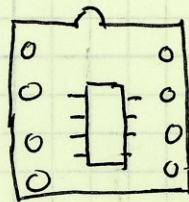

- Board has a ridge at top.
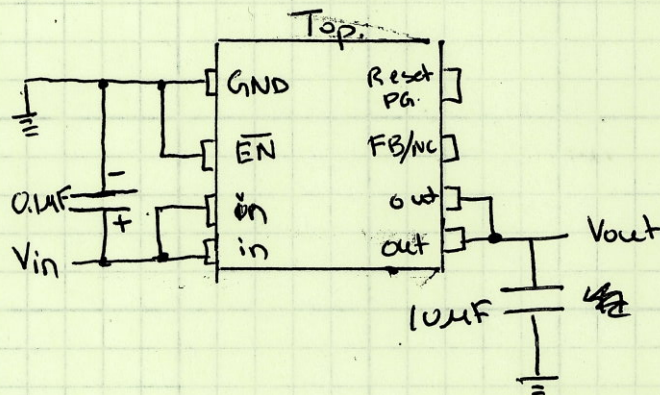
### Schematic

→ Regulator is a fixed 3.3 V version so  $V_{in} = 5V$ .



- $10\mu F$  capacitor needed to stabilize the control loop.

- Regulator runs a loop to check if  $V_o$  is 3.3 or not.

→ Feedback sensing system.

Note:  $0.1\mu F$  input capacitor not required. It is there to clean up signal.